




How PDN Filters Affect EMC Performance

Istvan Novak, PhD, IEEE Life Fellow
Samtec

OUTLINE

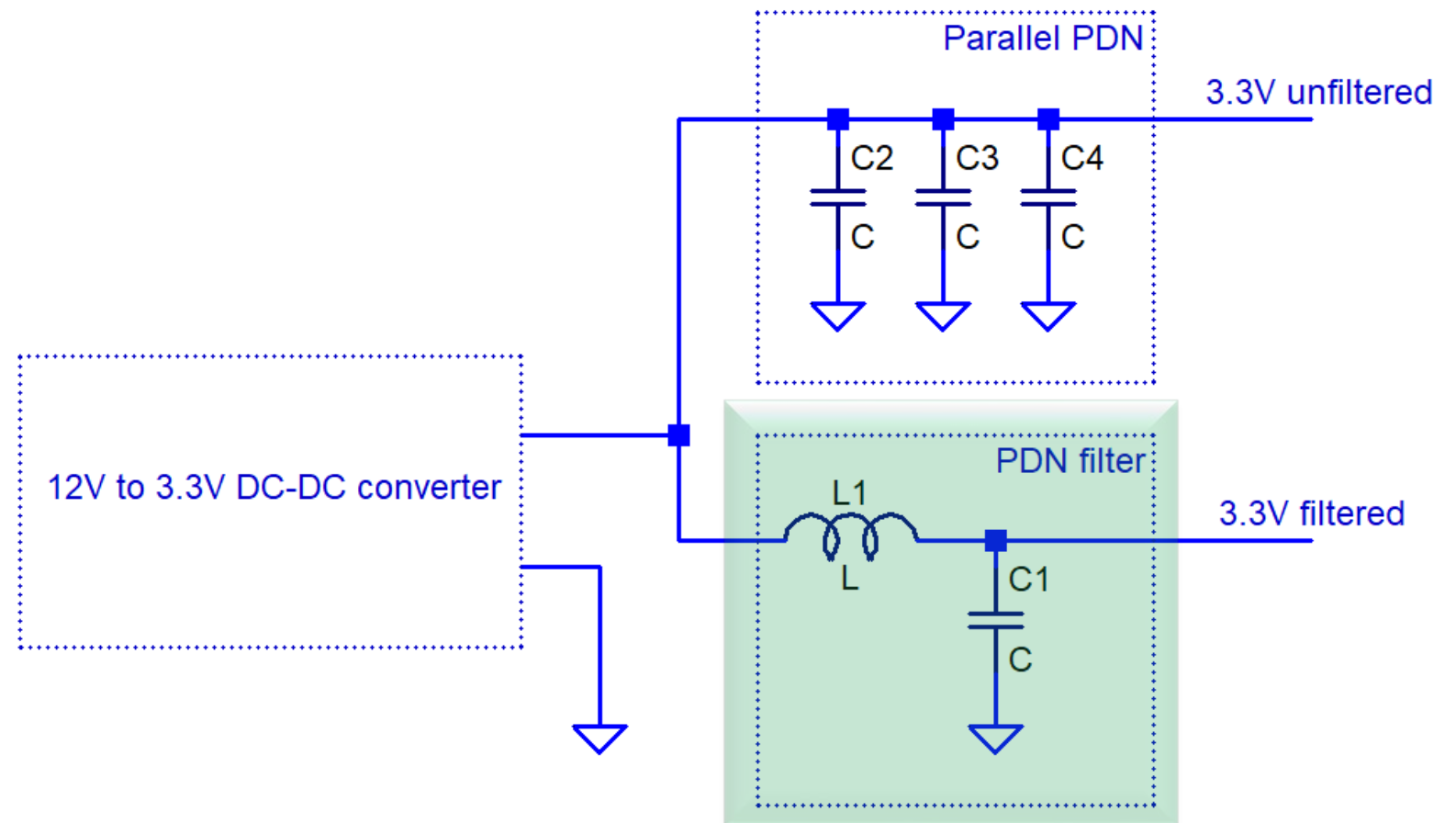- Background
- When we need a filter
- Typical noise sources
- Filter characteristics
- Filter illustrations
- Filter design process
- What can go wrong
- Summary
- Further reading



A Little EMC Background


EMC monitoring in 2020:



EMC monitoring station in the 70s:




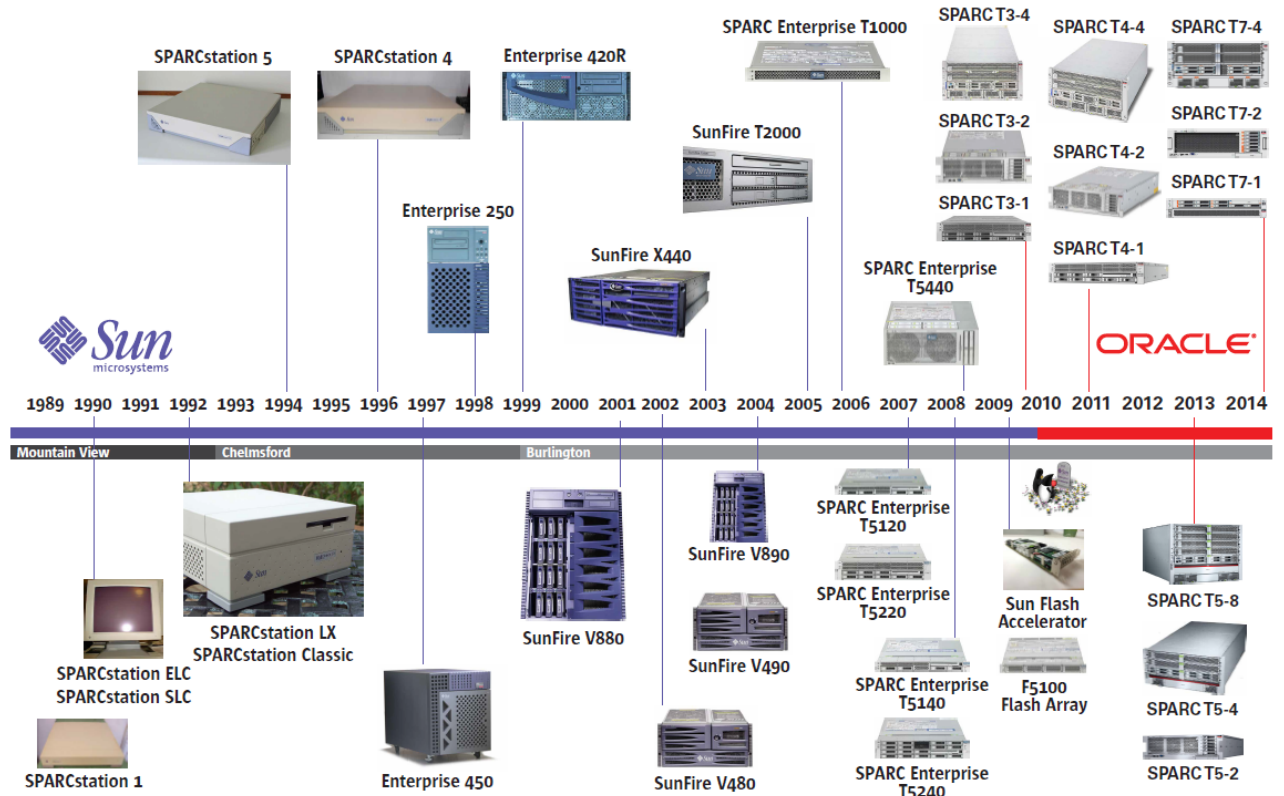Product portfolio commemorating Jeff Elsmore's career at SUN Microsystems – Oracle:



When We Need a Filter

To feed a sensitive low-current load

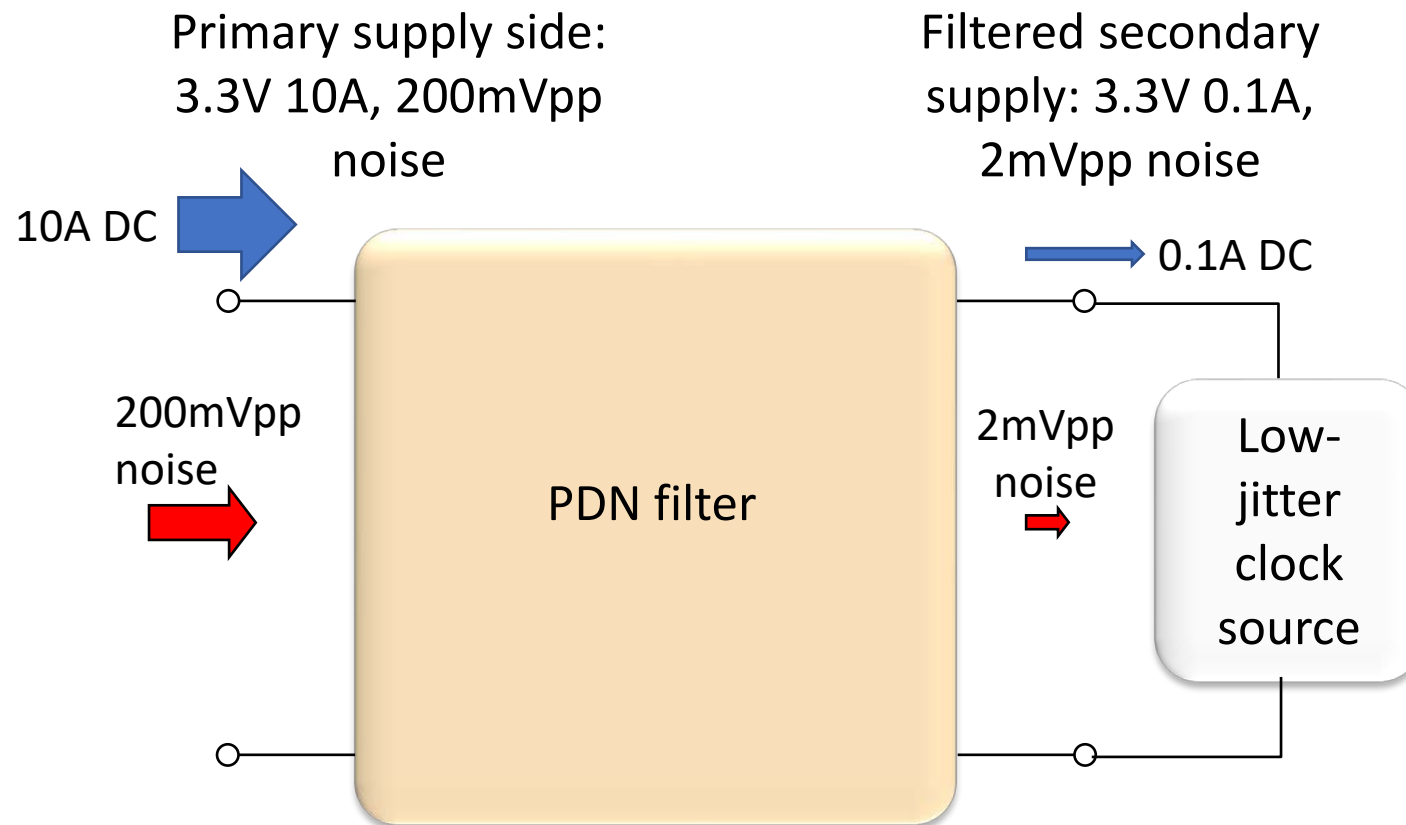


**Always ask yourself:
Do we need a filter
or not?**

It is easier to filter
for a low-current
rail than quiet a
high-current rail.

When We Need a Filter

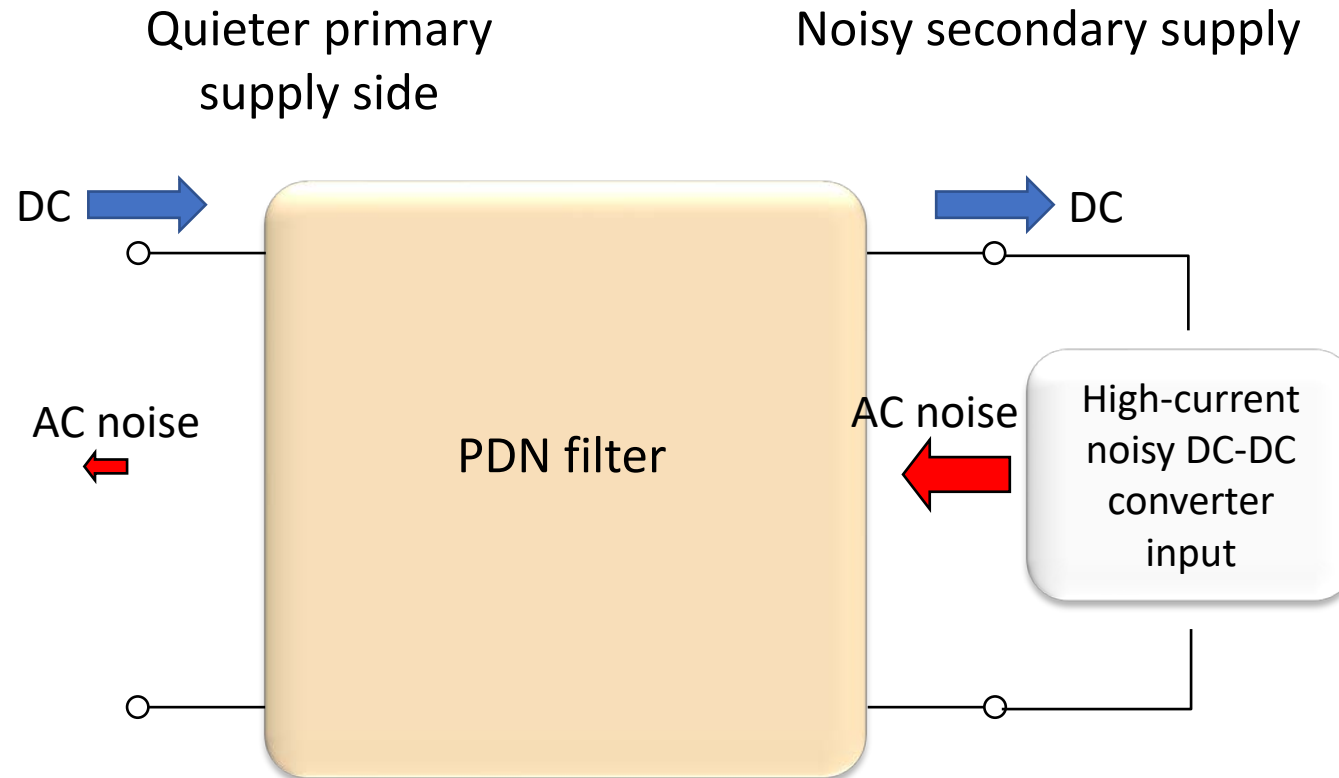To keep noise spilling out from noisy loads





**Always ask yourself:
Do we need a filter
or not?**

It is easier to contain noise at its source. Main stress parameter is capacitor ripple current.




Typical Noise Source

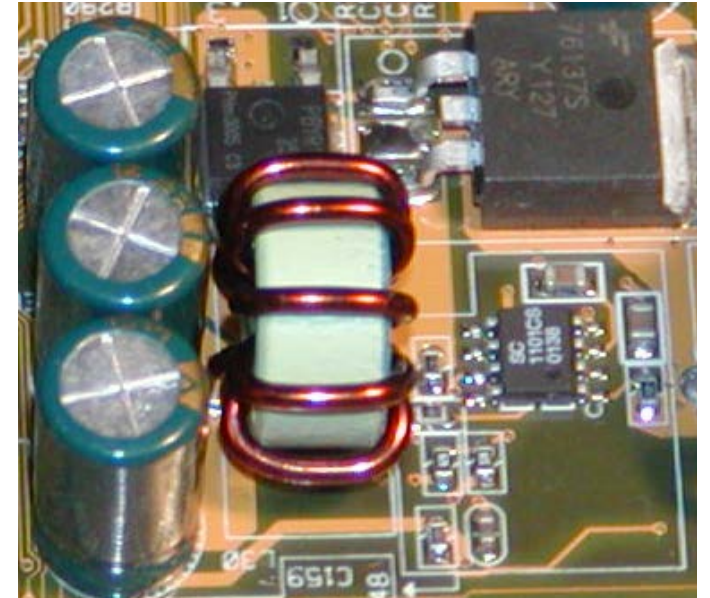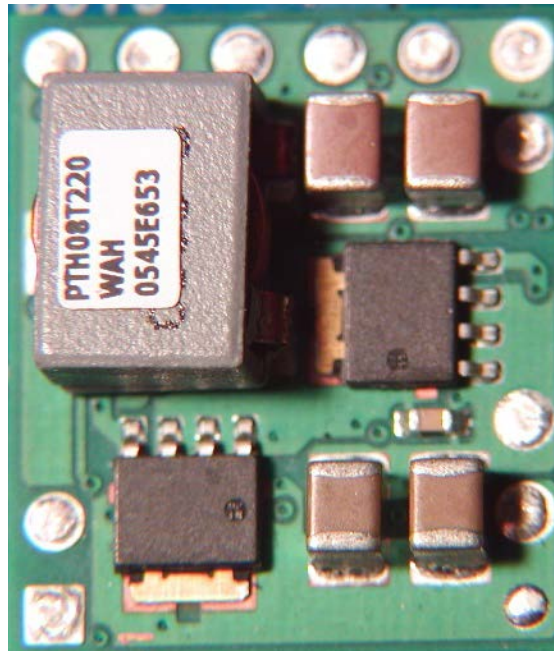- DC-DC converters are popular and needed for their high efficiency
- They tend to generate a lot of noise



DC-DC Converter Output Ripple Voltage

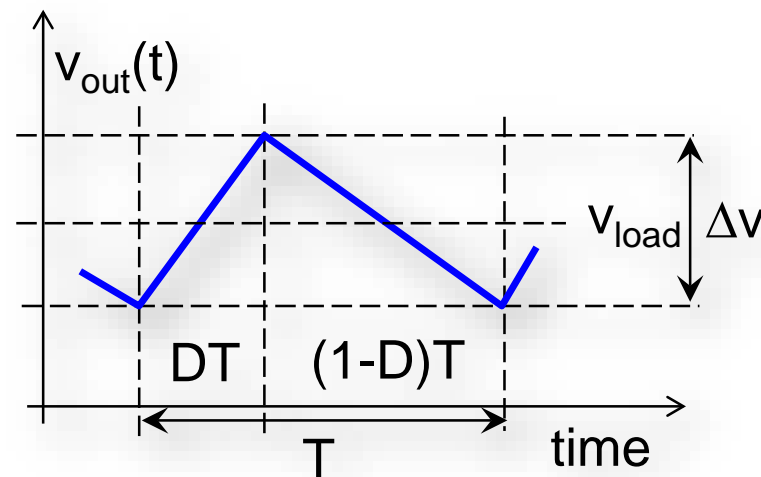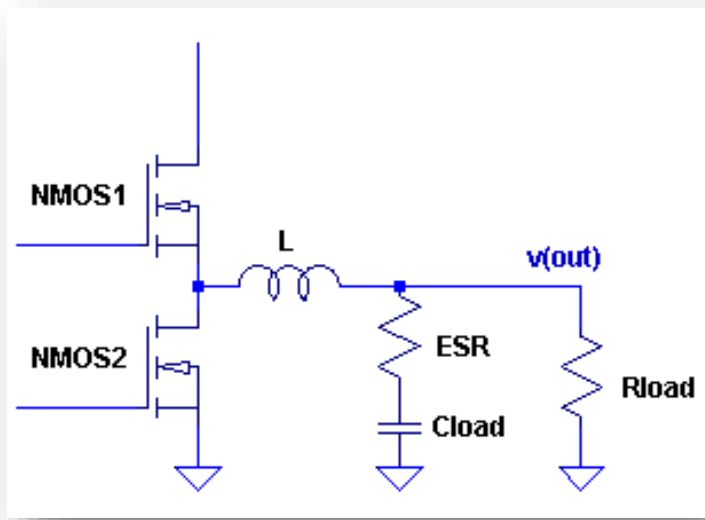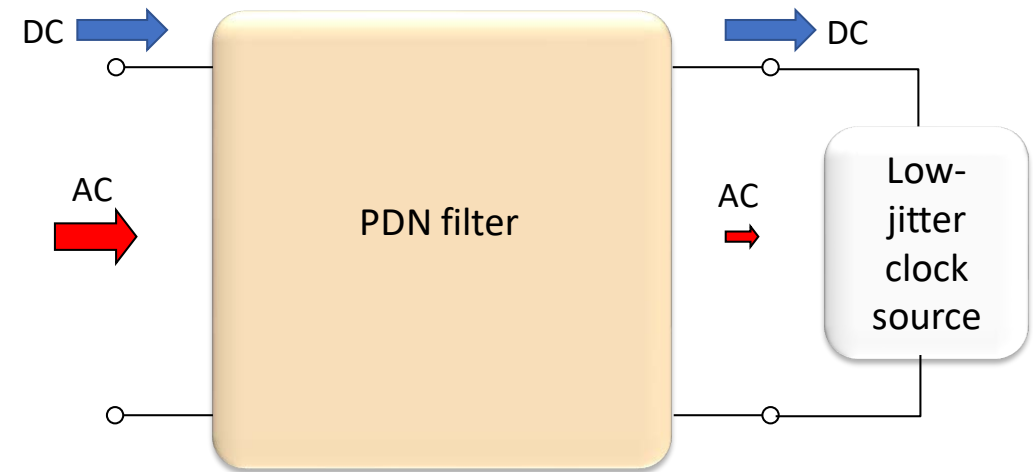- The inductor ripple current flows through the output capacitor
- First-order mid-frequency capacitor model = ESR-only
- Output ripple voltage shape closely follows inductor ripple current




If $C_{load} * ESR$ pole is below F_{sw} , the output ripple is:

$$\Delta v = ESR * \Delta I$$




DC-DC Converter Output Ripple Voltage

Time-domain harmonic composition of buck converter switching ripple

| OUTPUT CAPACITORS | | | | | Fmin [Hz] | Vin [V] | Fsw [Hz] | Sweep | D [%] | Ripple [mVpp] | m |
|-------------------|----------|----------|----------|----------|-----------|----------|----------|-------|-------------|-------------------|-----------|
| C [F] | 4.70E-04 | 4.70E-05 | 1.00E-05 | 1.00E-06 | 1.00E+03 | 12 | 5.00E+05 | 1 | 8.33 | 4.53 | 12.00 |
| R [Ohm] | 1.00E-02 | 3.00E-03 | 1.00E-02 | 1.00E+06 | Fmax [Hz] | Vout [V] | L | Max | delta_I [A] | Ripple est [mVpp] | Ratio [-] |
| L [H] | 2.00E-09 | 2.00E-09 | 1.00E-09 | 1.00E-09 | 1.00E+08 | 1 | 4.70E-07 | 10 | 3.9E+00 | 2.89 | 1.57 |
| N [-] | 3 | 3 | 10 | 0 | | | | | | | |

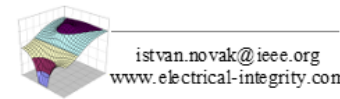




Number of periods
2

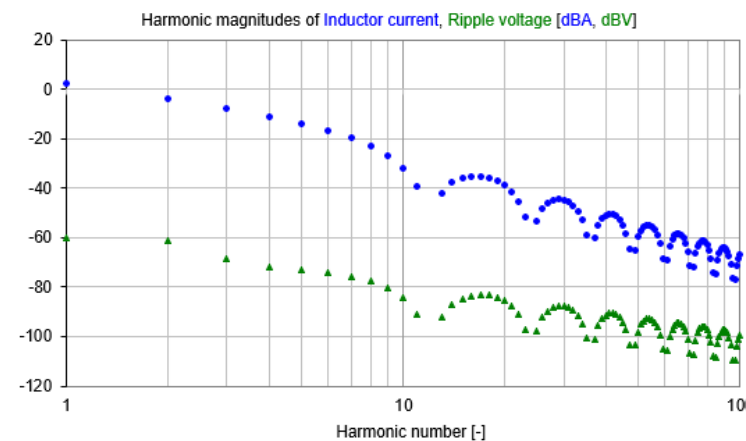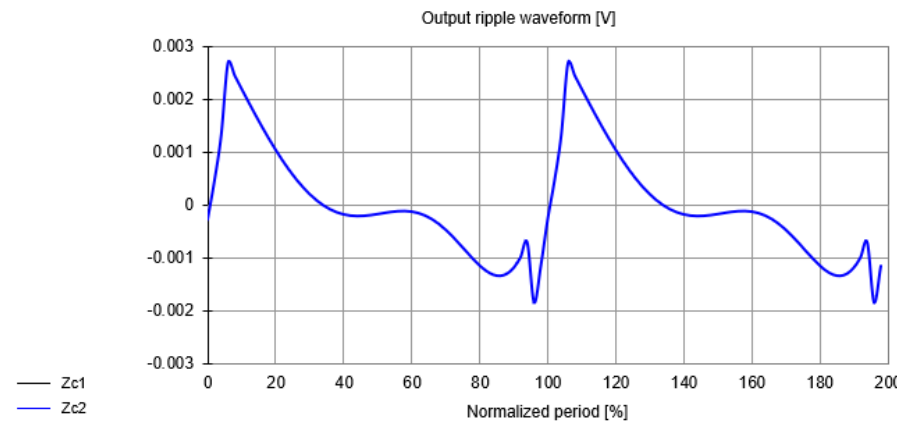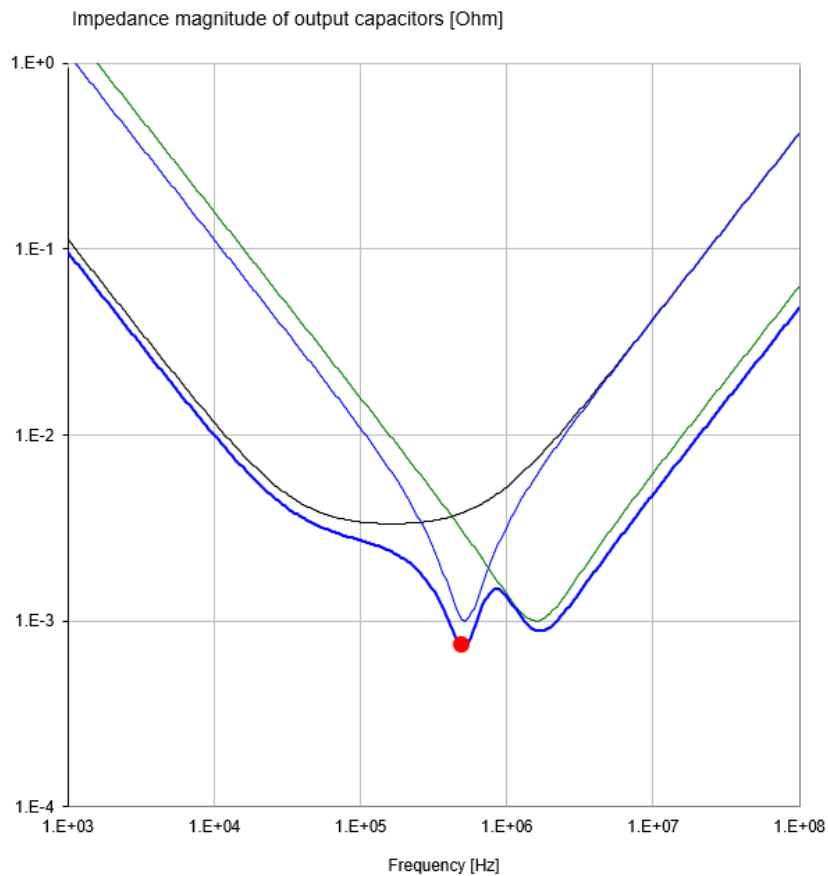

- The inductor ripple current flows through the output capacitor
- First-order mid-frequency capacitor model = ESR-only
- Output ripple voltage shape closely follows inductor ripple current



DC-DC Converter Input

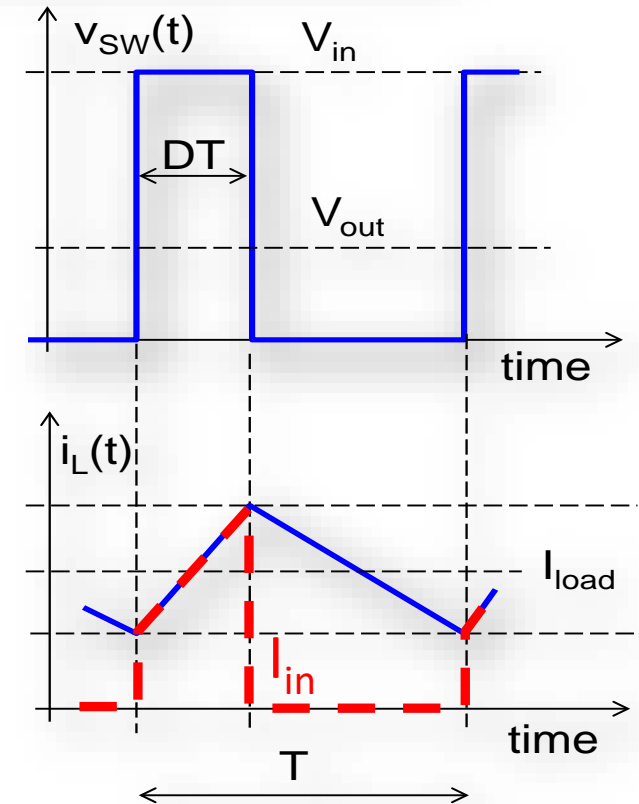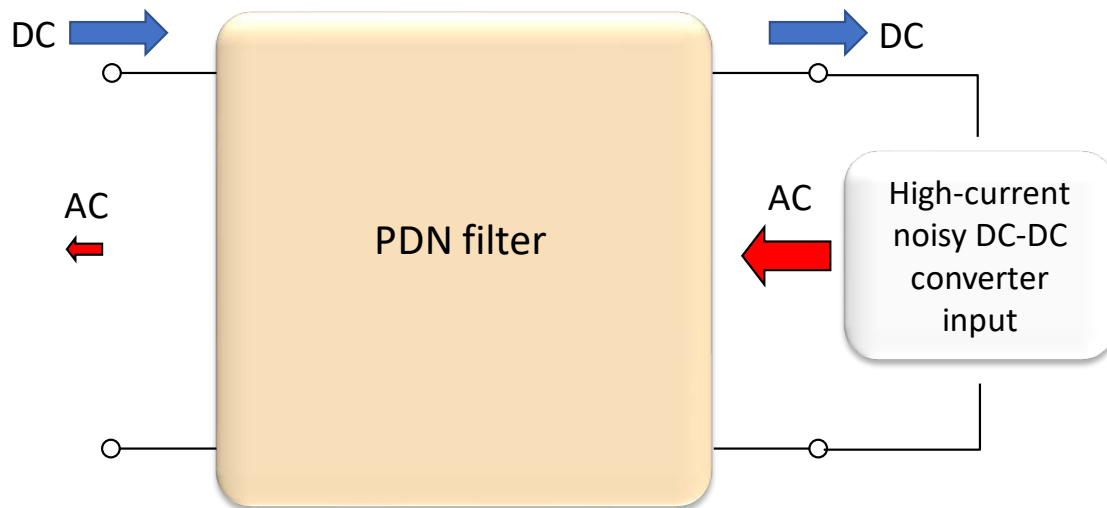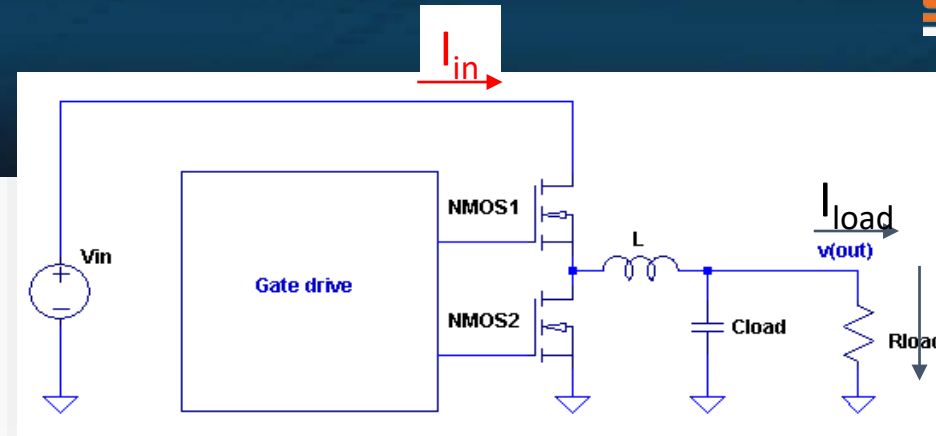- The input voltage is chopped by the switches
- Inductor current is continuous
- Input current has large jumps




DC-DC Converter Ringing

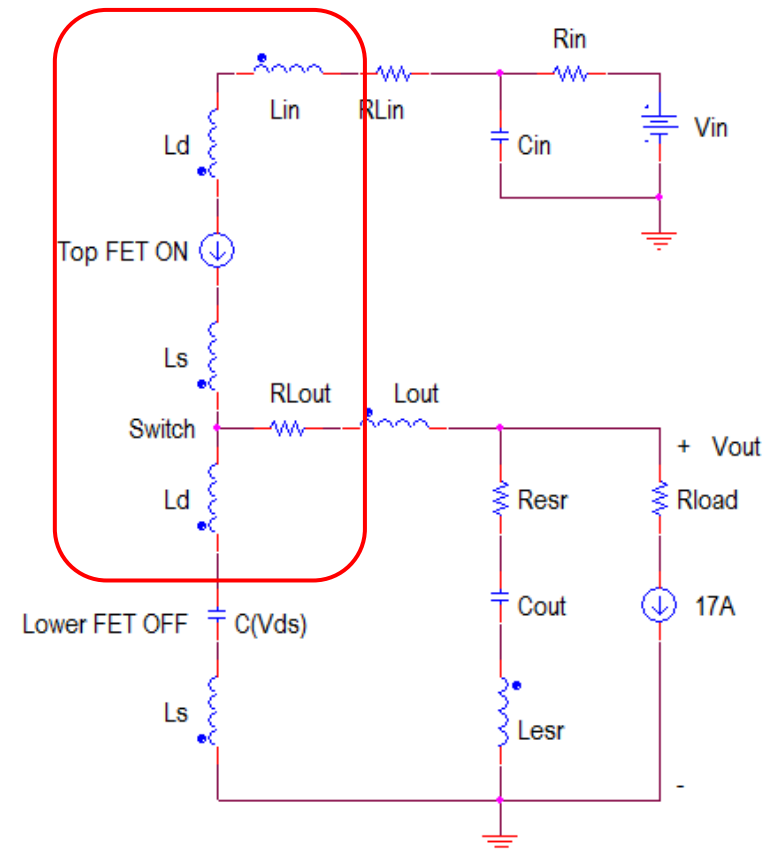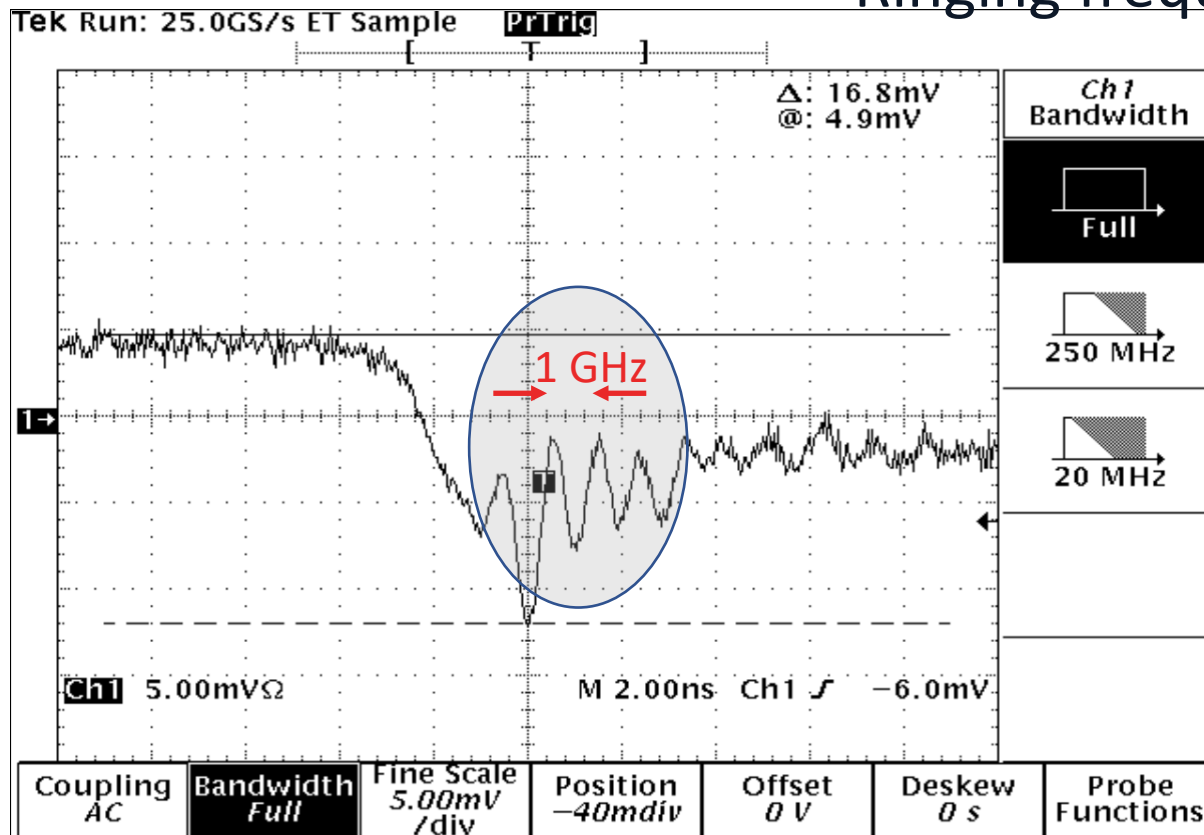- The switching edges may have high-frequency transients
- Ringing frequency: 50 – 1000 MHz



Source:
- Mid-Frequency Noise Coupling between DC-DC Converters and High-Speed Signals, DesignCon 2016
- What is New in DC-DC Converters; An OEM's Perspective, DesignCon 2012

Analog Supply Noise Filter (1)

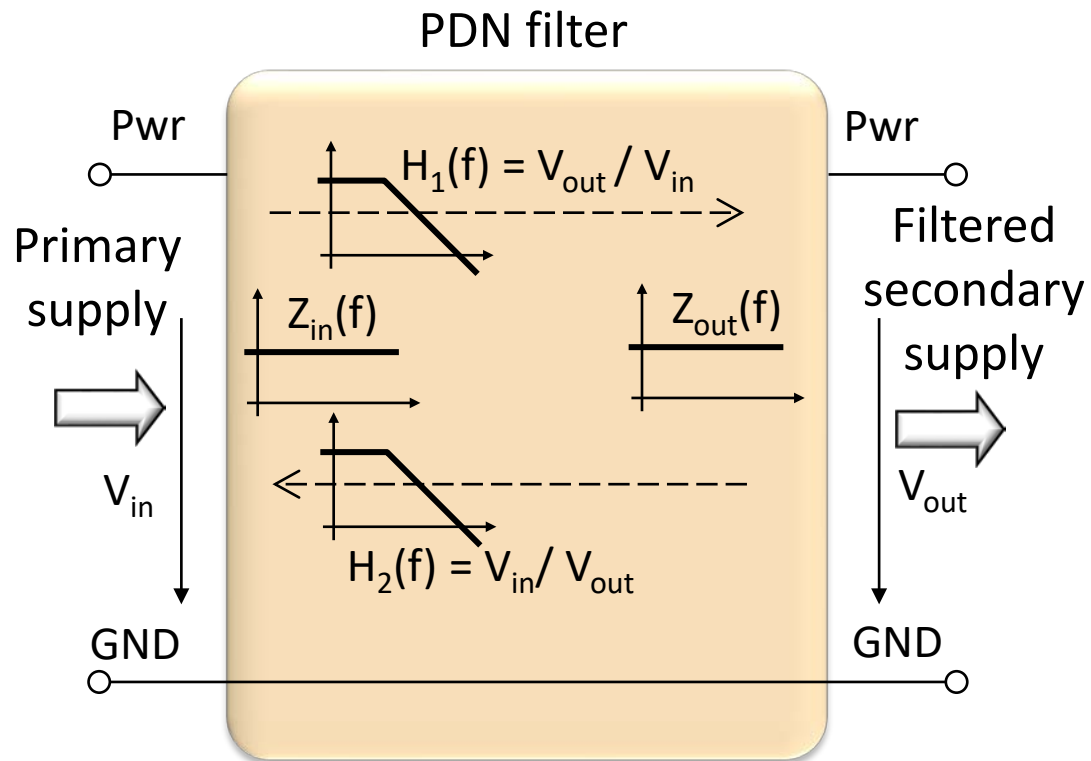

Possible functions and requirements:

- * Low-pass filtering from main to secondary
- * Low-pass filtering from secondary to primary
- * Output impedance for the load (*)
- * Input impedance for the source (*)

(*) Optional requirement

Passive filters may be physically symmetrical

Relevant transfer functions are mostly not symmetric





Watch DC voltage drops closely

Analog Supply Noise Filter (2)

* Use low-Q inductors or ferrites, or

* Low Dropout Regulators


* **DO NOT** use Hi-Q filters

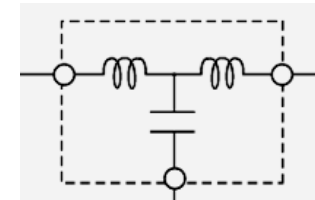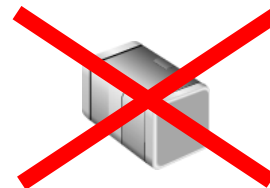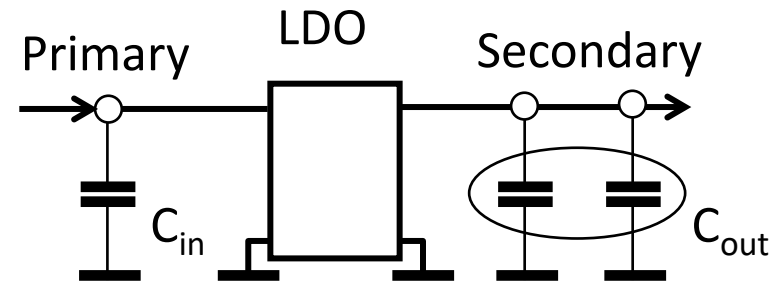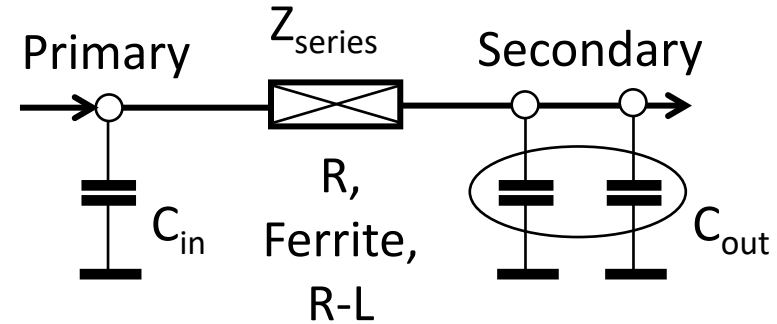

Transfer Functions


What transfer function matters?

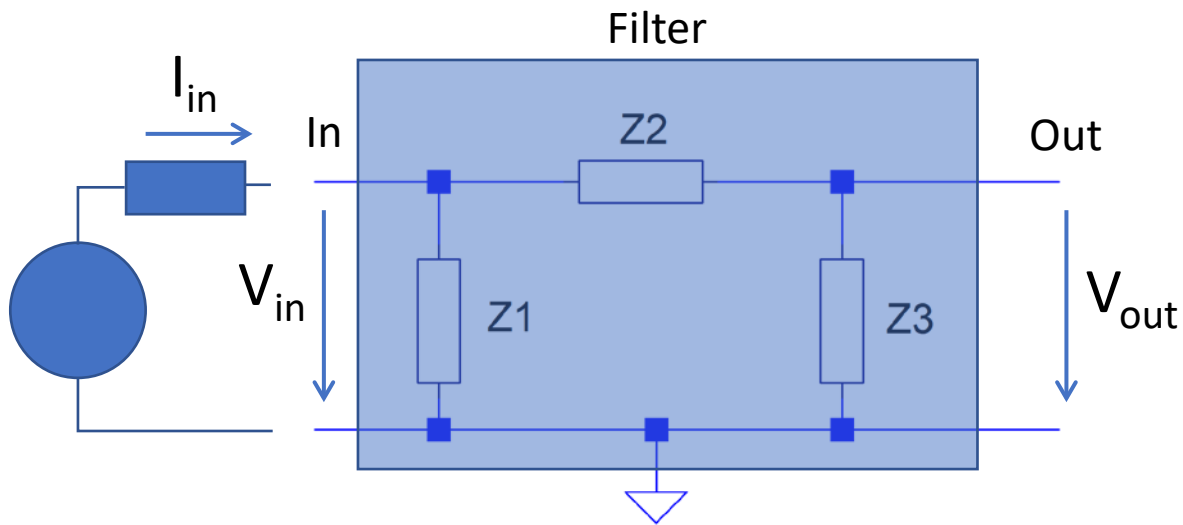- * Z_{21} or S_{21} ?
- * Something else?




$$Z_{21} = V_{out} / I_{in}$$
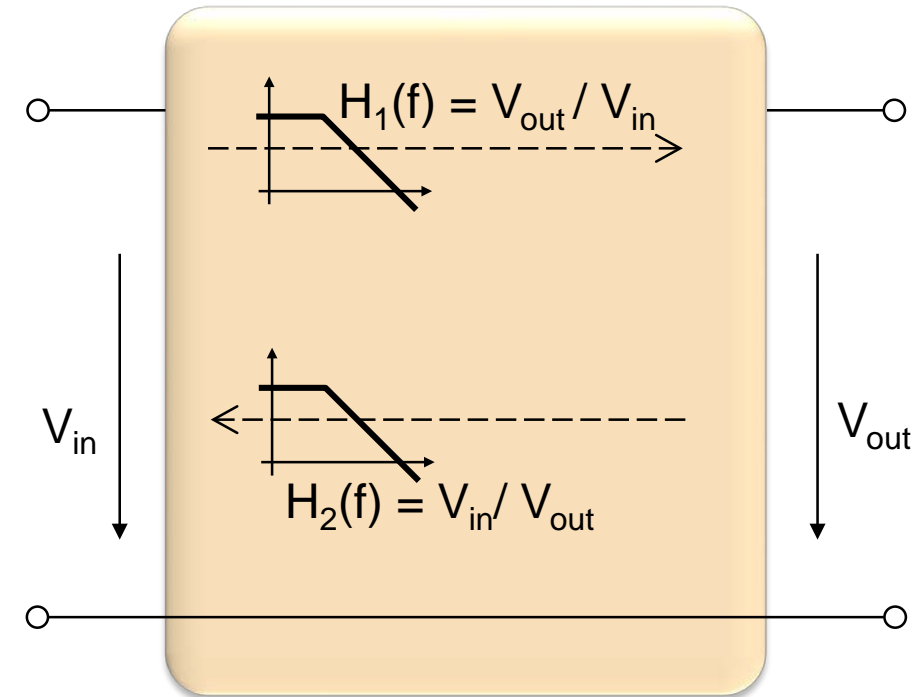
$$S_{21} = \text{wave}_{out} / \text{wave}_{in}$$



Transfer Functions

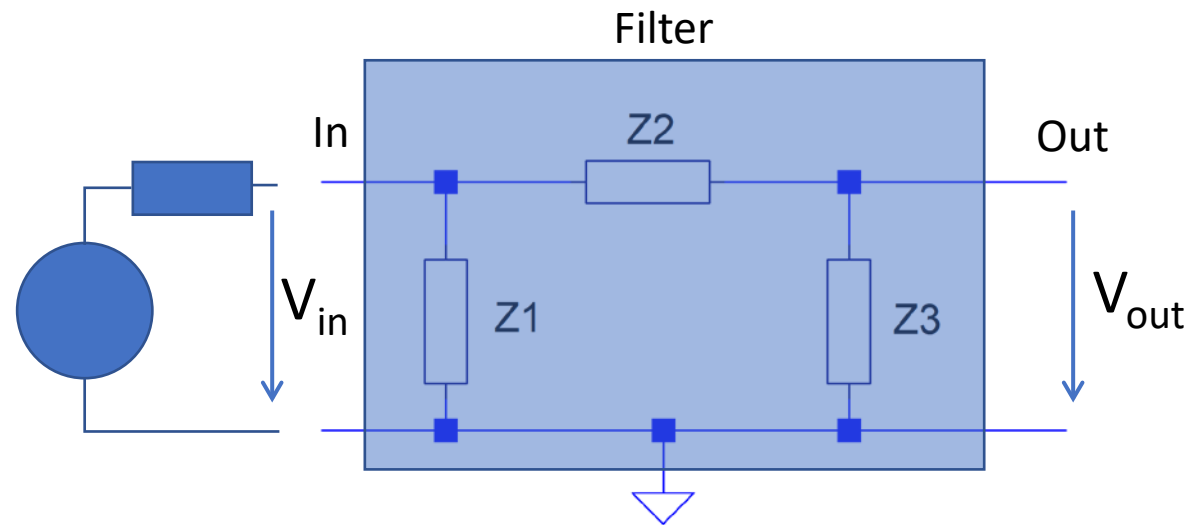For filters from a high-current to a low-current rail we need the *unloaded voltage transfer function*: V_{out} / V_{in}




Impedances



What filter impedance function matters?

- * Z_{11} , or Z_{22} ?
- * Something else?

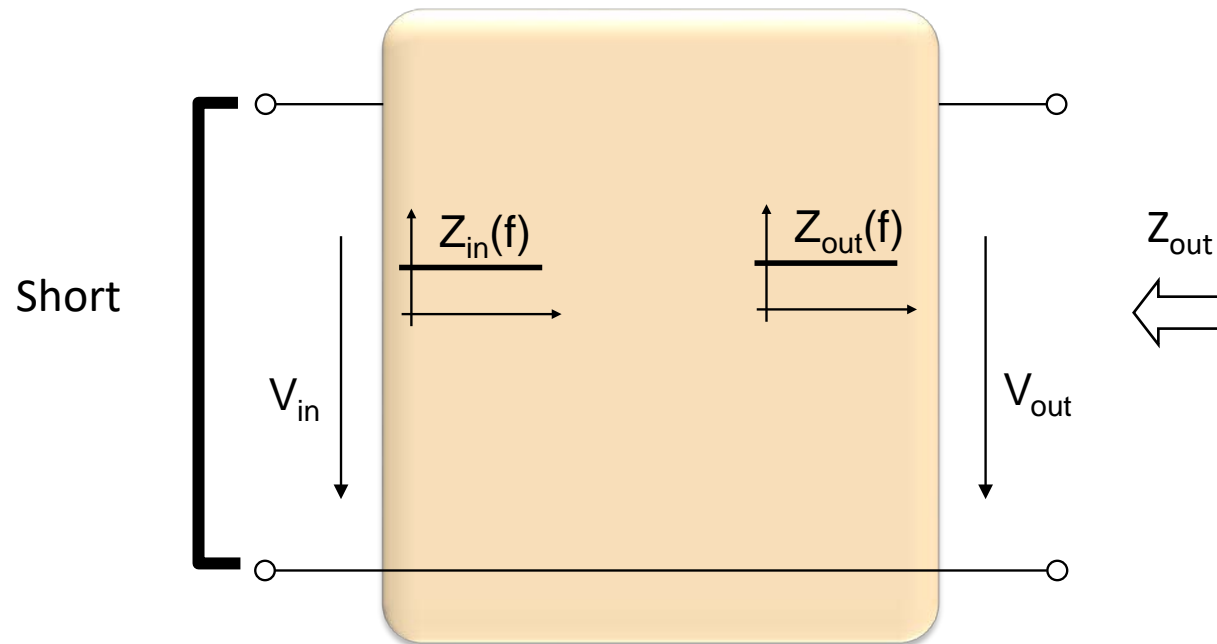For filters from a high-current to a low-current rail: *Output impedance with shorted input and input impedance with open output*



Filter Illustrations

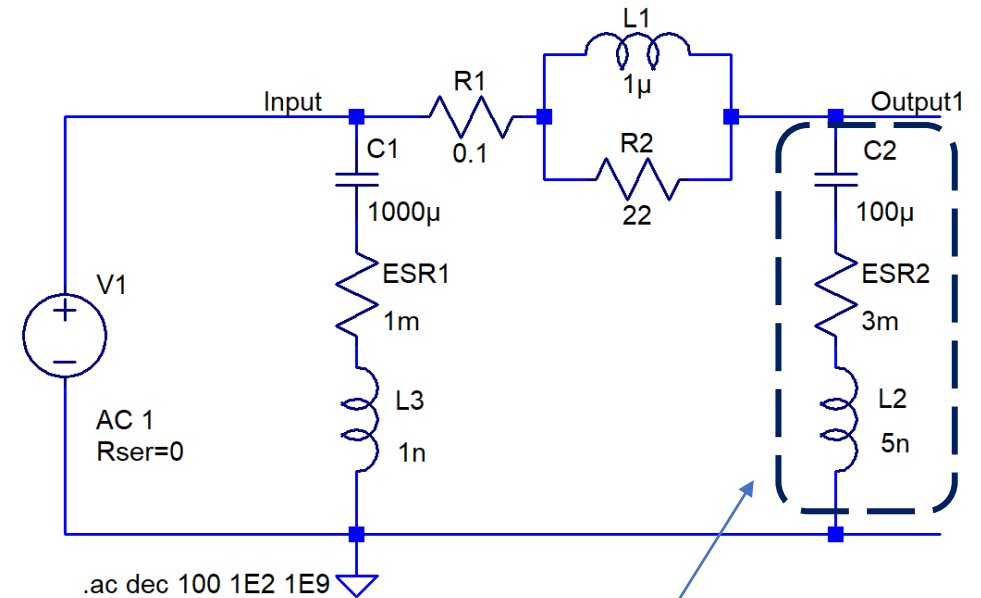
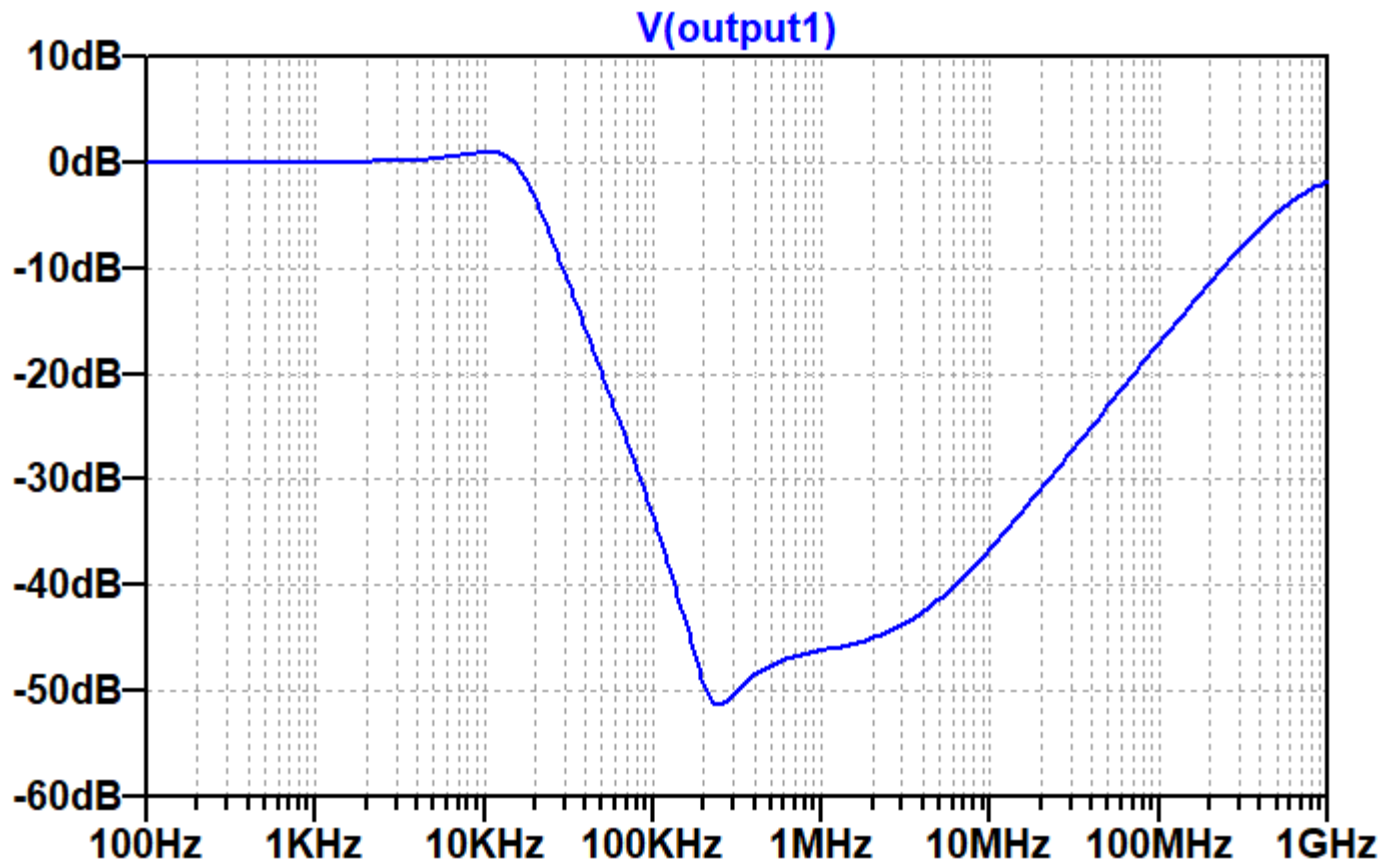


$C_{out}=C2$

100 µF 0.003 ohm 5 nH

Filter Illustrations, When More is Less

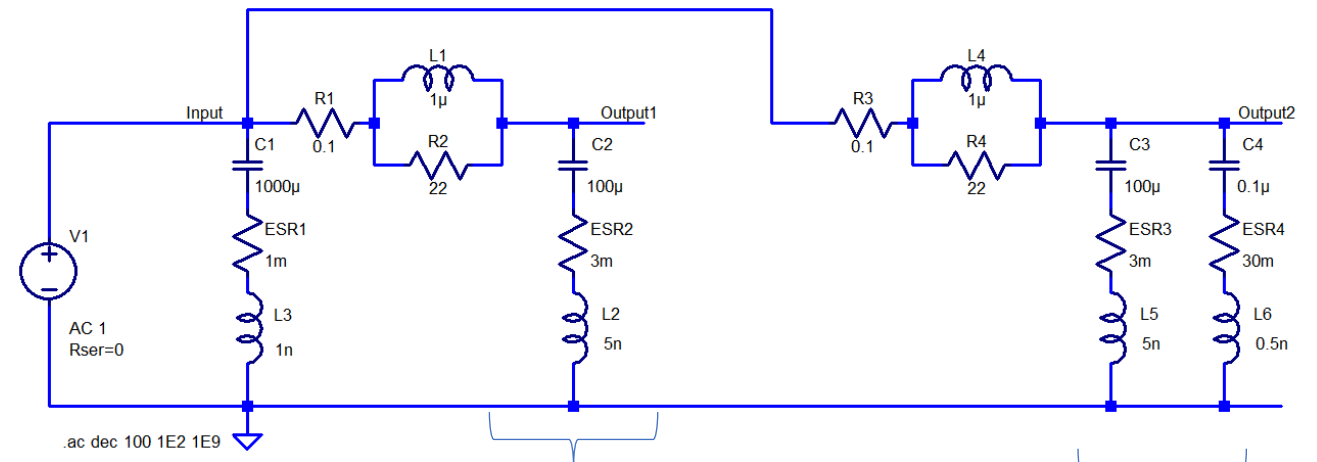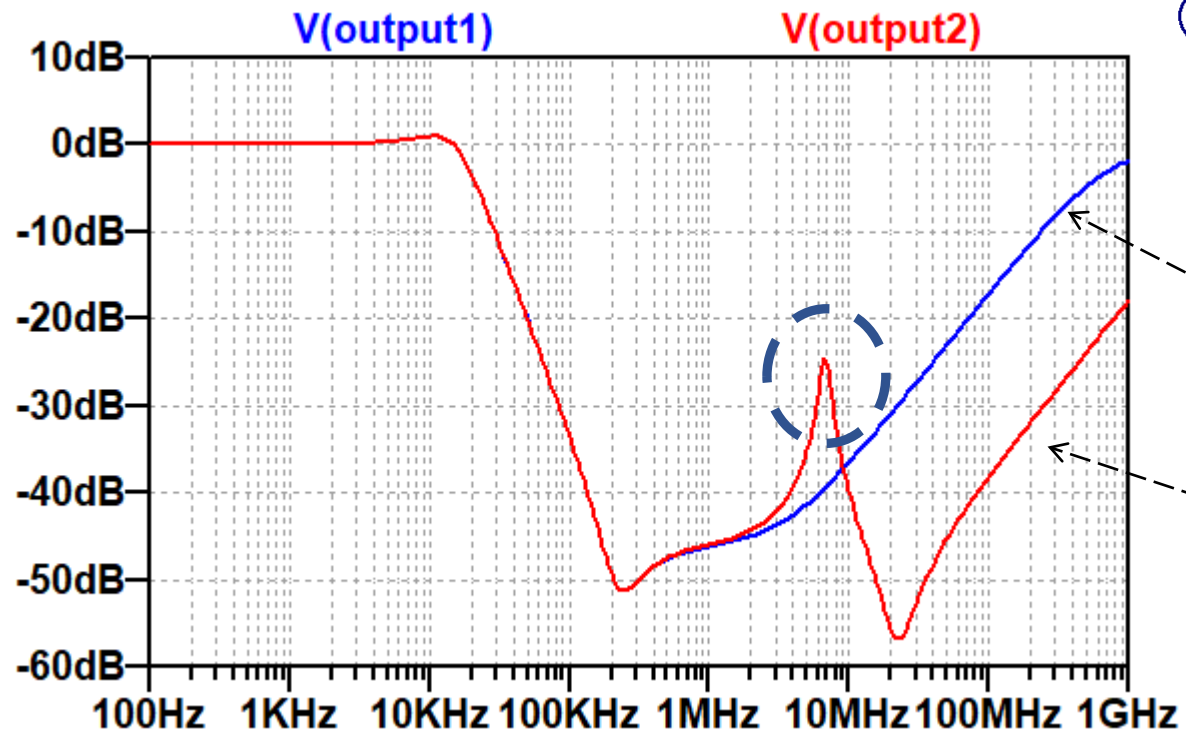Got better at high frequencies,
but we also got a peak





Case 1 C_{out}

Case 2 C_{out}

Case 1 C_{out}
100 μ F 0.003 ohm 5 nH

Case 2 C_{out}
100 μ F 0.003 ohm 5 nH
0.1 μ F 0.03 ohm 0.5 nH

Filter Illustrations, The Best

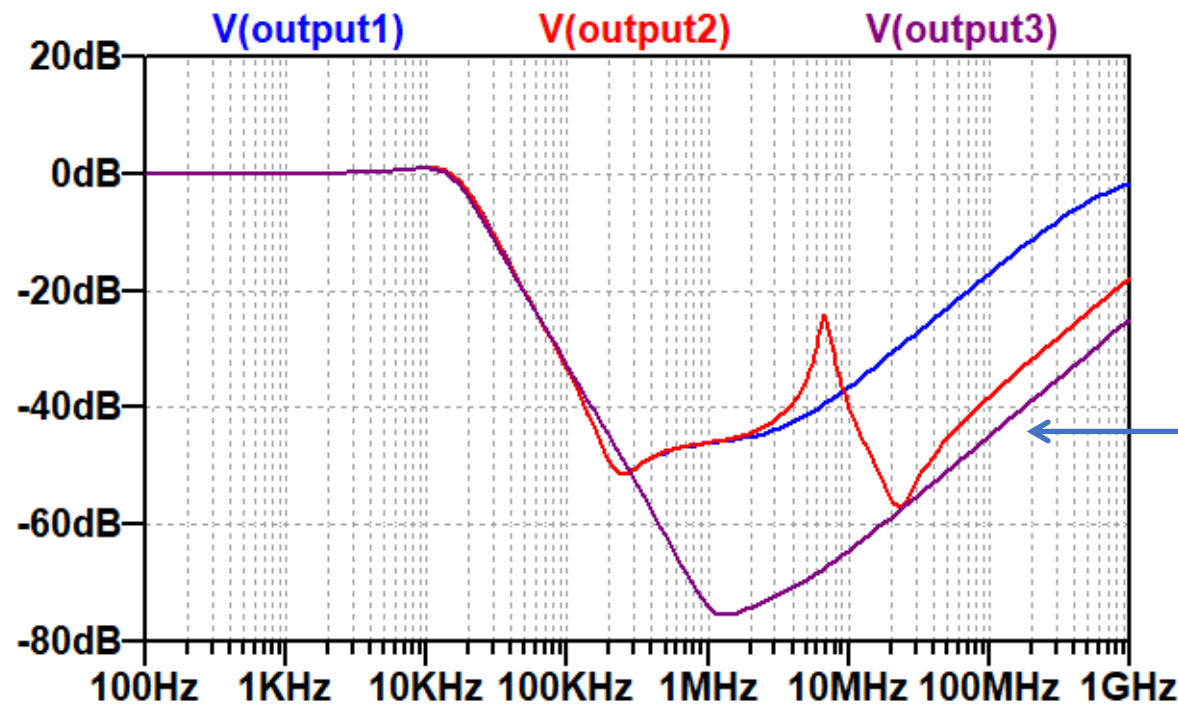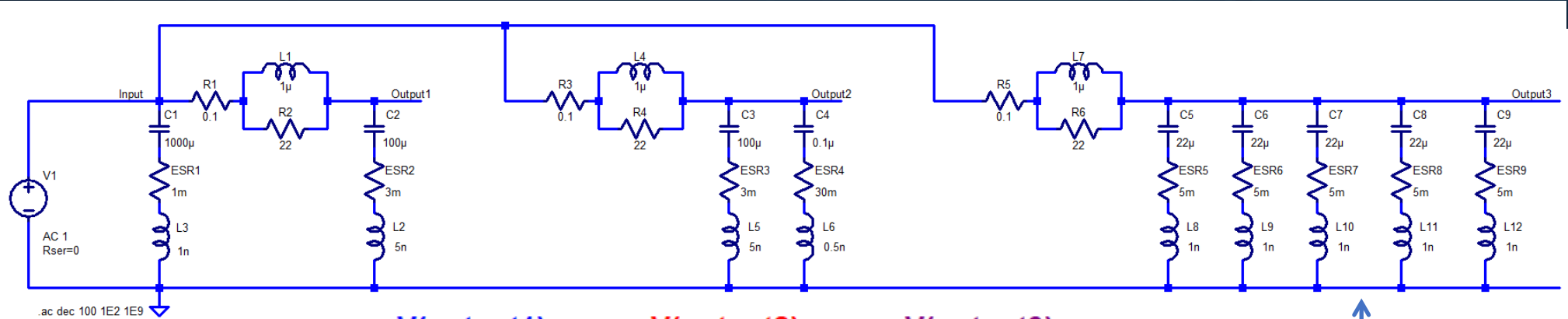


↑
Identical capacitors in parallel

The Filter Design Process

Collect input requirements

- * Offending frequency components (frequency, magnitude) to filter
- * Necessary attenuation
- * Set design parameters:
- * Filter cutoff frequency f_c and Q

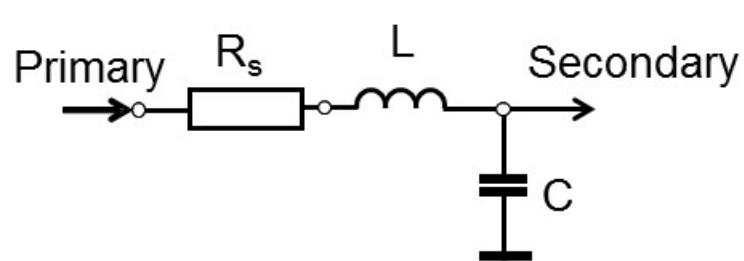Design the inductance and bulk capacitance based on:



$$f_c = \frac{1}{2\pi\sqrt{LC}}, \quad Q = \frac{\sqrt{L}}{R_s C}$$

Or use a circuit simulator to quickly iterate component values...

Low-Current Filter Example (1)


Design requirements for low-current filter

- * Cutoff frequency $f_c = 100$ kHz (DC-DC converter running at 1MHz)
- * $Q = 0.5$

Assume $R_s = 1$ Ohm


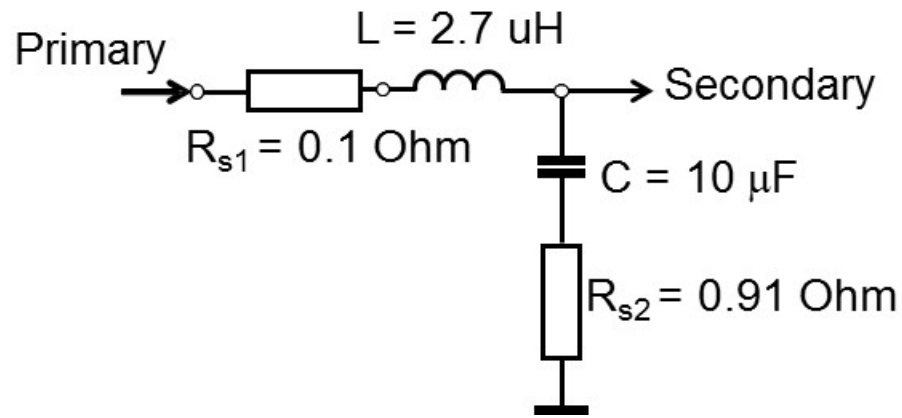
$$f_c = \frac{1}{2\pi\sqrt{LC}}, \quad Q = \frac{\sqrt{L}}{R_s C}$$




Calculated values:

- * $L = 2.7 \mu\text{H}$
- * $C = 10 \mu\text{F}$

Select:

- * $L = 2.7 \mu\text{H}$ 0.1 Ohm
- * $C = 10 \mu\text{F}$ + 0.91 Ohm

Low-Current Filter Example (2)

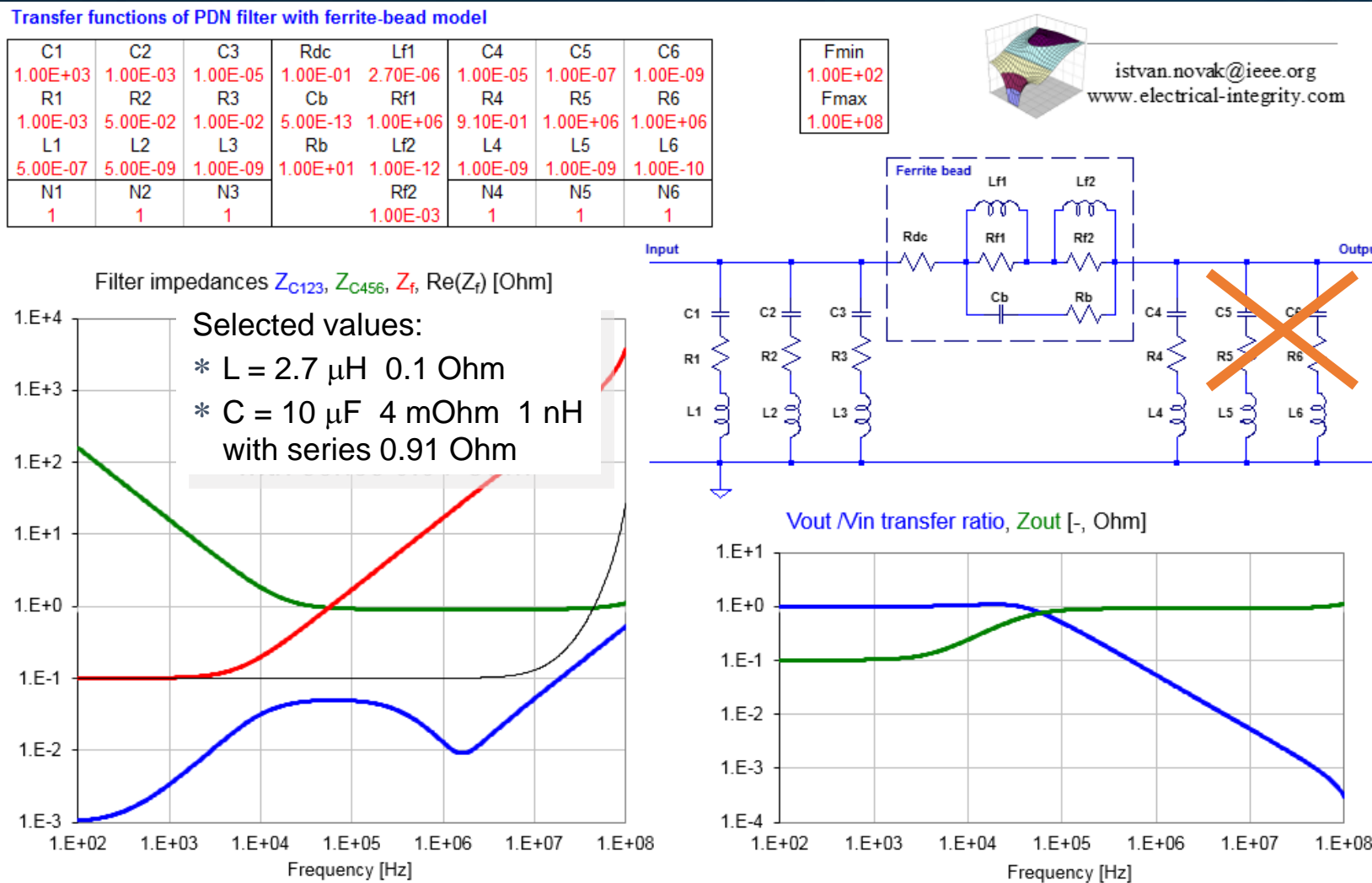

http://www.electrical-integrity.com/Tool_download_files/PDN-filter_WExcel2016-32-64b_v06.xlsm

Low-Current Filter Example (3)

Selected components:

- * Coilcraft 181PS-272 L = 2.7 μ H
0.08 Ohm
- * Kemet C0805C106K4PAC C =
10 μ F 4 mOhm 1 nH

The screenshot shows the Coilcraft website interface. On the left, the 'Power Inductor Finder Results' section displays a table of search results for a 2.7 μ H inductor. The table includes columns for Part number, Mount, Core material, Other*, L (μ H), DCR (Ω), I sat (A), I rms (A), L max (mm), W max (mm), H max (mm), and Price @ 1,000. The results are sorted by footprint and DCR.


| Part number | Mount | Core material | Other* | L (μ H) | DCR (Ω) | I sat (A) | I rms (A) | L max (mm) | W max (mm) | H max (mm) | Price @ 1,000 |
|--------------|--------|---------------|--------|--------------|------------------|-----------|-----------|------------|------------|------------|---------------|
| 1812PS-272 | SM | Ferrite | S | 2.7 | 0.0800 | 1.4 | 2.3 | 5.87 | 4.98 | 3.81 | \$0.83 |
| DO1608C-272 | SM | Ferrite | | 2.7 | 0.0800 | 2.1 | 2.45 | 6.60 | 4.45 | 2.92 | \$0.64 |
| XAL7030-272 | SM | Composite | S | 2.7 | 0.0173 | 12.8 | 11.4 | 8.00 | 8.00 | 3.10 | \$0.87 |
| RFB0807-2R7 | Leaded | Ferrite | | 2.7 | 0.0140 | 5.5 | 6.54 | 8.80 | 8.80 | 7.50 | \$0.30 |
| MSS1038T-252 | SM | Ferrite | S | 2.5 | 0.0100 | 9.26 | 6.65 | 10.50 | 10.20 | 4.00 | \$0.55 |

On the right, a 'Ceramic Type / Voltage / Capacitance' selection tool is shown. It includes sections for 'Chip Style' (Standard Chips and High Voltage Chips), 'Dielectric Type' (COG, X7R, X5R, X8R, G, R, P, H, Y5V, Z5U, X8L, V, N), and 'Rated Voltage' (2VDC to 10000VDC). A 'Capacitance List' shows various capacitor values, with '10 μ F - C0805C106K4PAC' selected. A 'Done' button is visible at the bottom right.

- All filter components may be impacted by bias stress
 - Capacitance loss due to voltage bias
 - Inductance loss due to current bias
- The filter has to pass DC current and therefore very low frequency noise can not be eliminated
 - Sub-harmonic converter ripple
 - Out-of-band spurious signals
 - Low frequency random noise
- Series resistive loss maintains second-order filtering; resistance in the parallel path approaches first-order filtering
- Check the DC-DC converter operating frequency before you switch to a different converter!

Be Aware


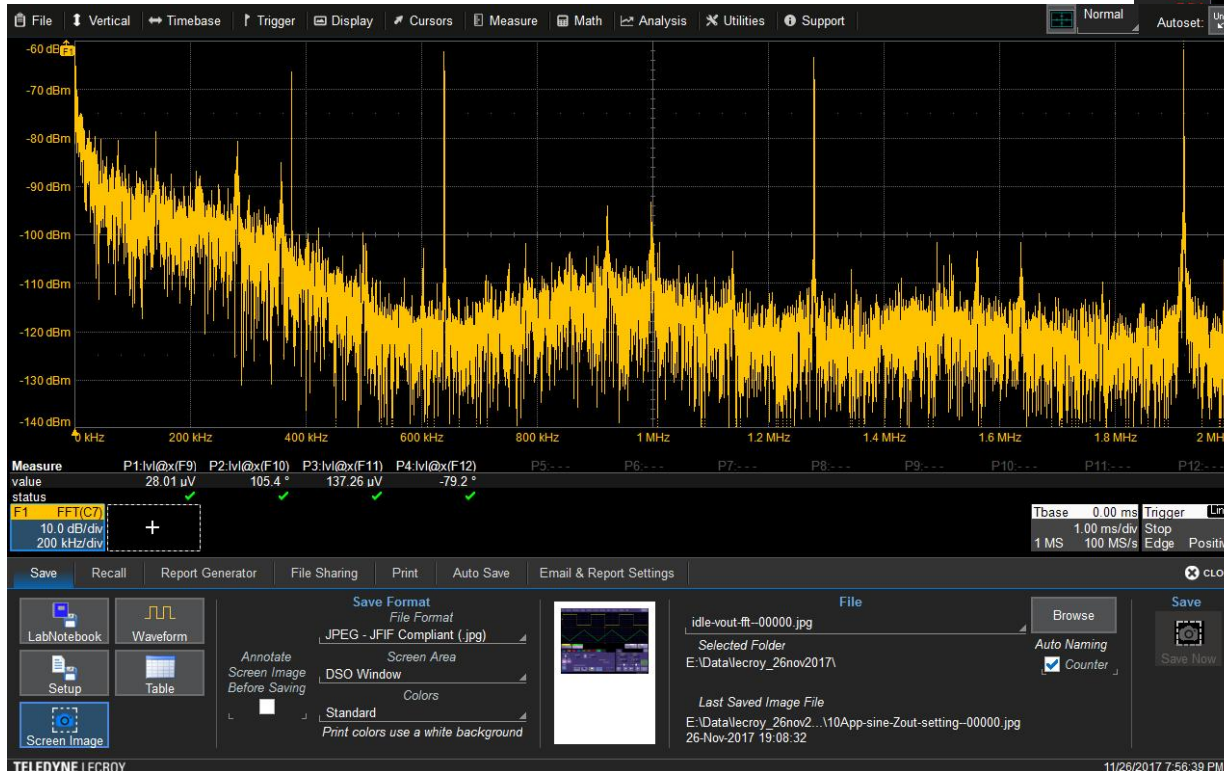
- Random wander of current sharing
- 600 kHz switching frequency
- Six-phase 12V to 0.9V regulator



Current sharing among phases in the time domain
Spectrum of output voltage

http://www.electrical-integrity.com/Paper_download_files/DC18_PAPER_MeasuringCurrentAndSharing_corrected_v3.pdf




Be Aware, Distribution of Losses

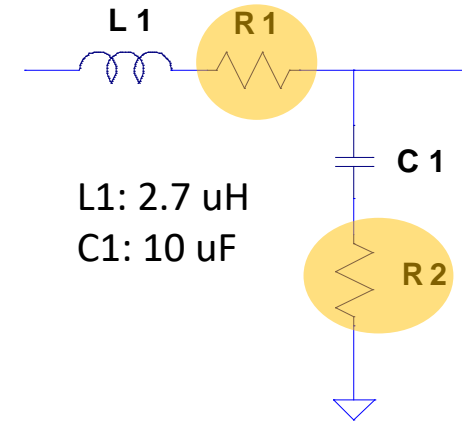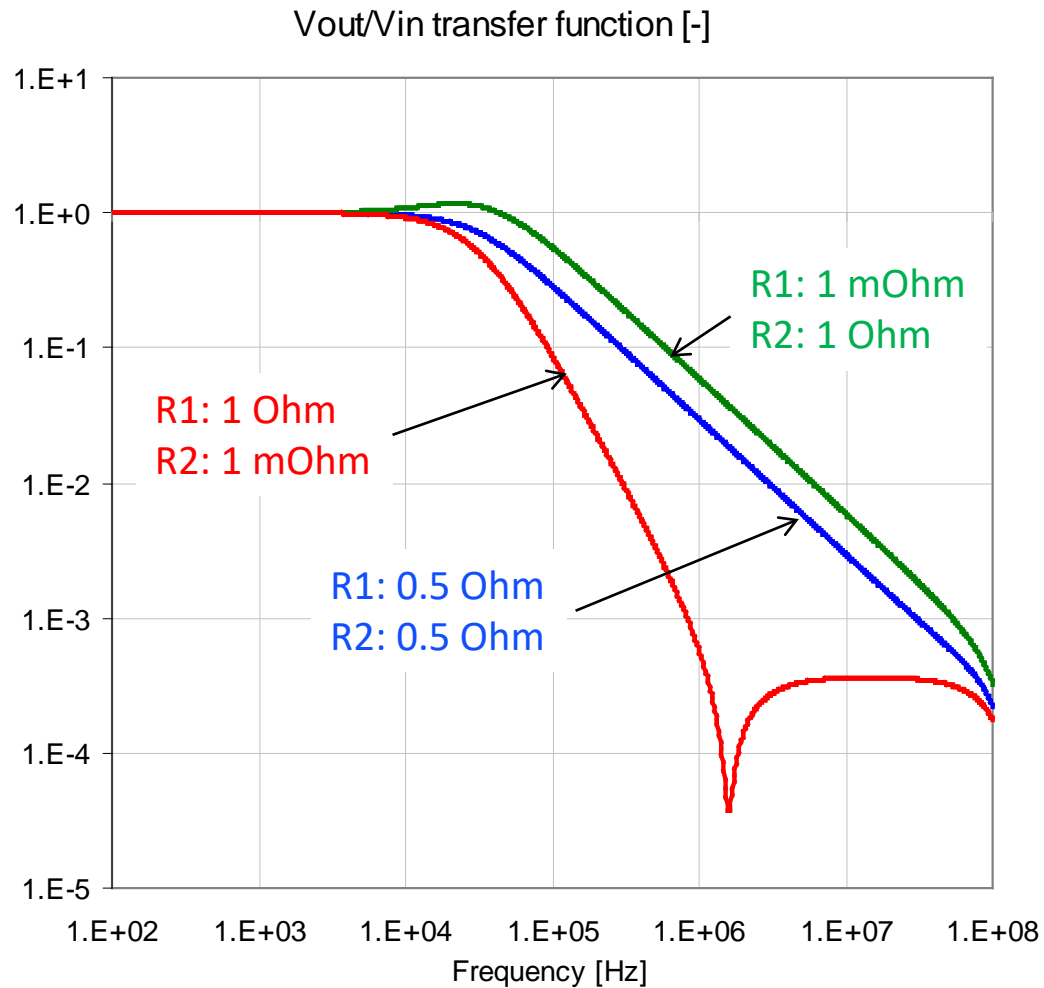

Series resistive loss maintains second-order filtering; resistance in the parallel path approaches first-order filtering

Be Aware, Bias Effects

9dB peaking at 25 kHz!

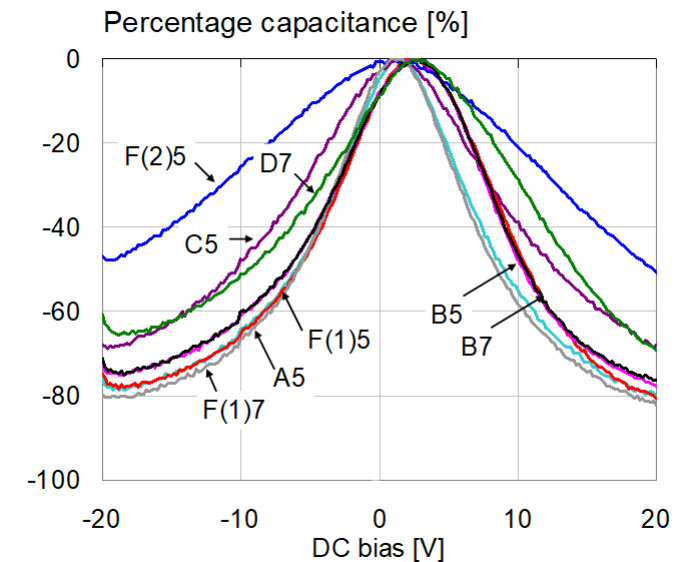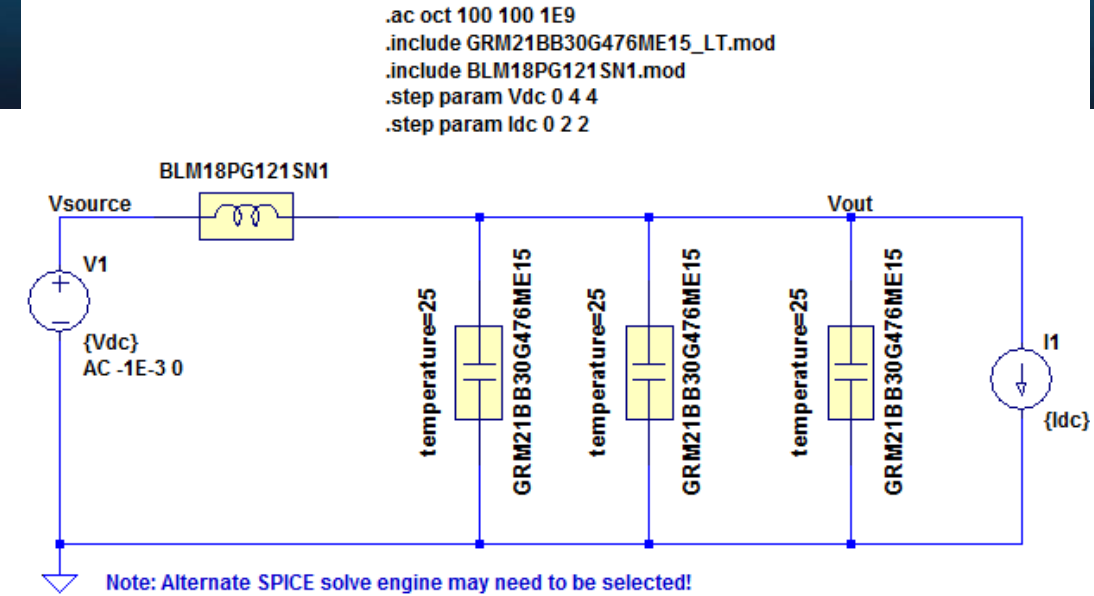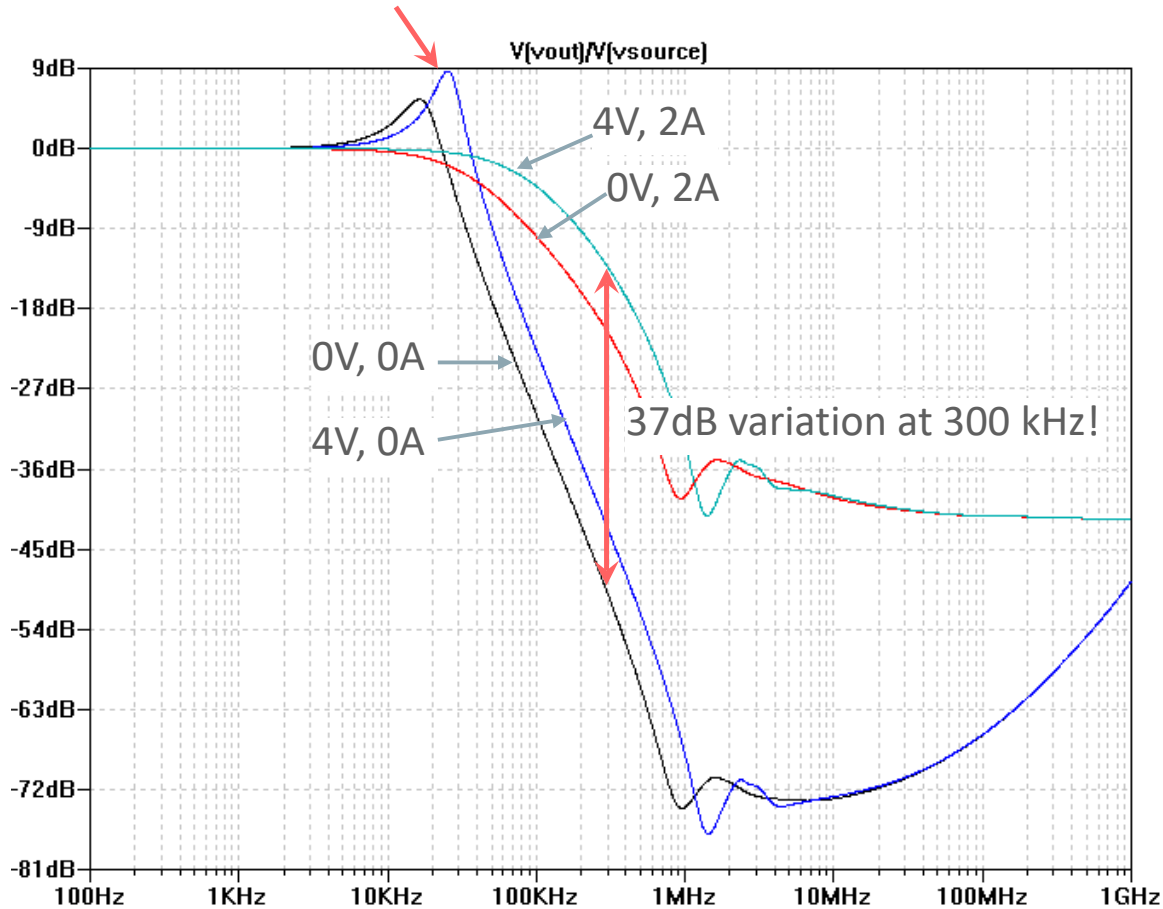

Source: "How Much Capacitance Do We Really Get?,"
 QuietPower columns, http://www.electrical-integrity.com/Quietpower_files/QuietPower-40.pdf

Loss of Capacitance in MLCCs

| | Percentage range [%] | Relative multiplier |
|----------------------|----------------------|---------------------|
| Initial tolerance | +/-10 | 0.9 ... 1.1 |
| Temperature effect | +/-15 | 0.85 ... 1.15 |
| DC bias effect | +0 -70 | 0.3 ... 1 |
| AC bias effect | +0 -30 | 0.7 ... 1 |
| Aging (over 3 years) | +0 -7.5 | 0.925 ... 1 |


- * For worst case, have to multiply all multipliers
- * High CV ceramic capacitors can lose up to 85% of capacitance
- * Highest impact is DC and AC bias voltage


0.15 **1.27**


Source: "How Much Capacitance Do We Really Get?," QuietPower columns, http://www.electrical-integrity.com/Quietpower_files/QuietPower-40.pdf

In-System Interference

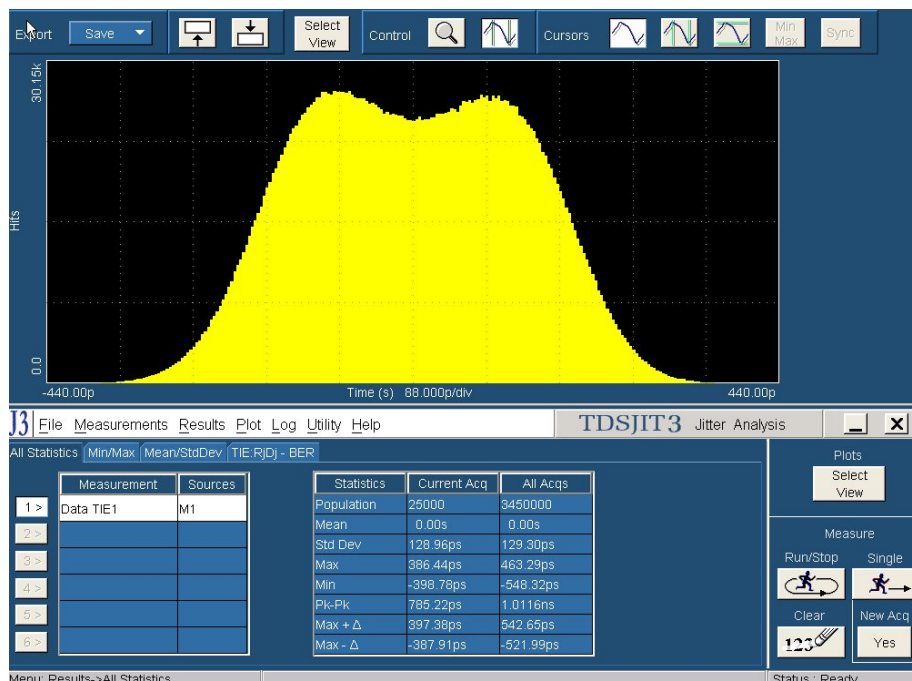GbE jitter measured on a live system
Only the AC/DC power supply was changed



With PSU #1

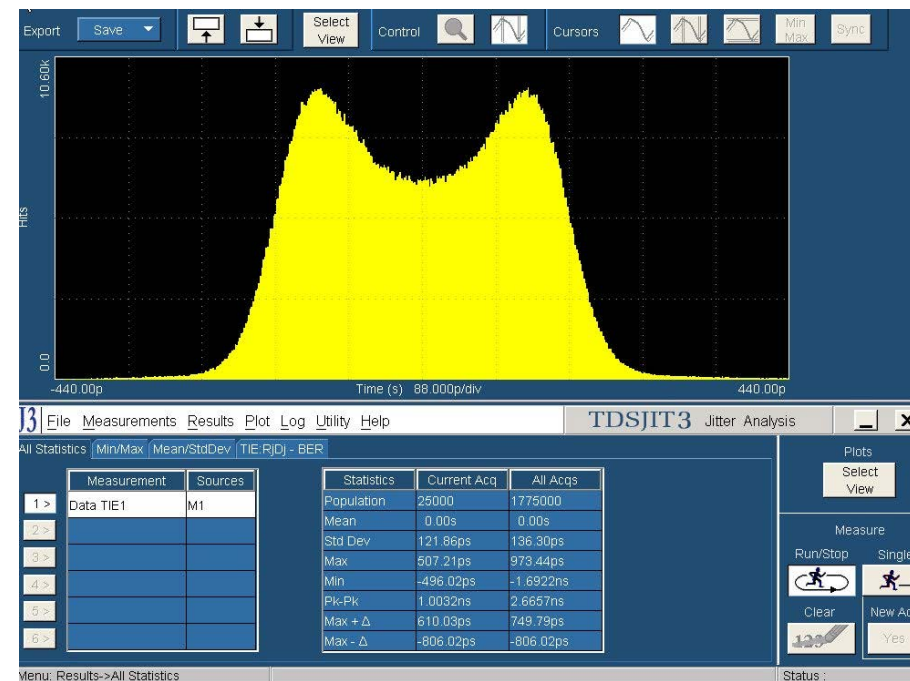

With PSU #2

http://www.electrical-integrity.com/Paper_download_files/DC18_PAPER_MeasuringCurrentAndSharing_corrected_v3.pdf

The First EMC-SMOG Map of Earth

Live interactive map is at

<https://gnd.bme.hu/mb/site>

Credit:

- Spectrum data from Hungarian SMOG-P nanosatellite, <http://gnd.bme.hu/smog>
- Visualization and data processing: Markotics Boldizsar and Takacs Donat, BME Cosmos Society, <https://kozmosz.space/>



Summary

- **Filters can effectively suppress noise propagating from**
 - High-power source to low-power sensitive circuit
 - High-current load transients spilling back out to main supply rails
- **Primary design goals for LC filters**
 - Provide enough attenuation of the offending spectrum
 - Avoid peaking of transfer function that would amplify instead of attenuating the noise
- **But**
 - Series filter reactance must be balanced by capacitance after the filter
 - If the filter is not needed or incorrectly implemented, it can create problems
- **Filter performance can be impacted by bias current (loss of inductance) and voltage (loss of capacitance)**

Further Resources

“How to Design Good PDN Filters,” DesignCon 2019, January 29-31, 2019, Santa Clara, CA

http://www.electrical-integrity.com/Paper_download_files/DC19_Tutorial_SLIDES_HowToDesignGoodPDNFilter.pdf

“Do You Really Need that Ferrite Bead in the PDN?”

http://www.electrical-integrity.com/Quietpower_files/QuietPower-55.pdf

For illustration tools, papers, blogs, SI and PI courses, see

<http://www.electrical-integrity.com/>



THANK YOU

Istvan.Novak@samtec.com

Istvan.Novak@ieee.org